

## Lab 4-Classwork Part 2

19-02-2020

CS 254-Digital Logic Design Lab

14:00-16:55

The following digital circuits must be designed using VHDL, and simulated and tested using Quartus.


- Q4. (5marks) Design a 2-bit Grey to BCD converter using Decoder and Demultiplexers only (Use Demultiplexers to make the basic gates required)

Grey Code( $G_1G_0$ )	BCD(ABCD)
00	0000
01	0001
11	0010
10	0011

The trace file format for the design is as follows:

 **$G_1G_0$  ABCD**

- BONUS**(5marks) Design a 8:3 Priority encoder using two 4:2 Priority encoders and Demultiplexers only (Use Demultiplexers to make the basic gates required)



Input									Output			
En	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	X	Y	Z	V
0	X	X	X	X	X	X	X	X	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	1
1	X	1	0	0	0	0	0	0	0	0	1	1
1	X	X	1	0	0	0	0	0	0	1	0	1
1	X	X	X	1	0	0	0	0	0	1	1	1
1	X	X	X	X	1	0	0	0	1	0	0	1
1	X	X	X	X	X	1	0	0	1	1	0	1
1	X	X	X	X	X	X	1	0	1	0	1	1
1	X	X	X	X	X	X	X	1	1	1	1	1

The trace file format for the design is as follows:

**EnD<sub>0</sub>D<sub>1</sub>D<sub>2</sub>D<sub>3</sub>D<sub>4</sub>D<sub>5</sub>D<sub>6</sub>D<sub>7</sub> XYZV**