
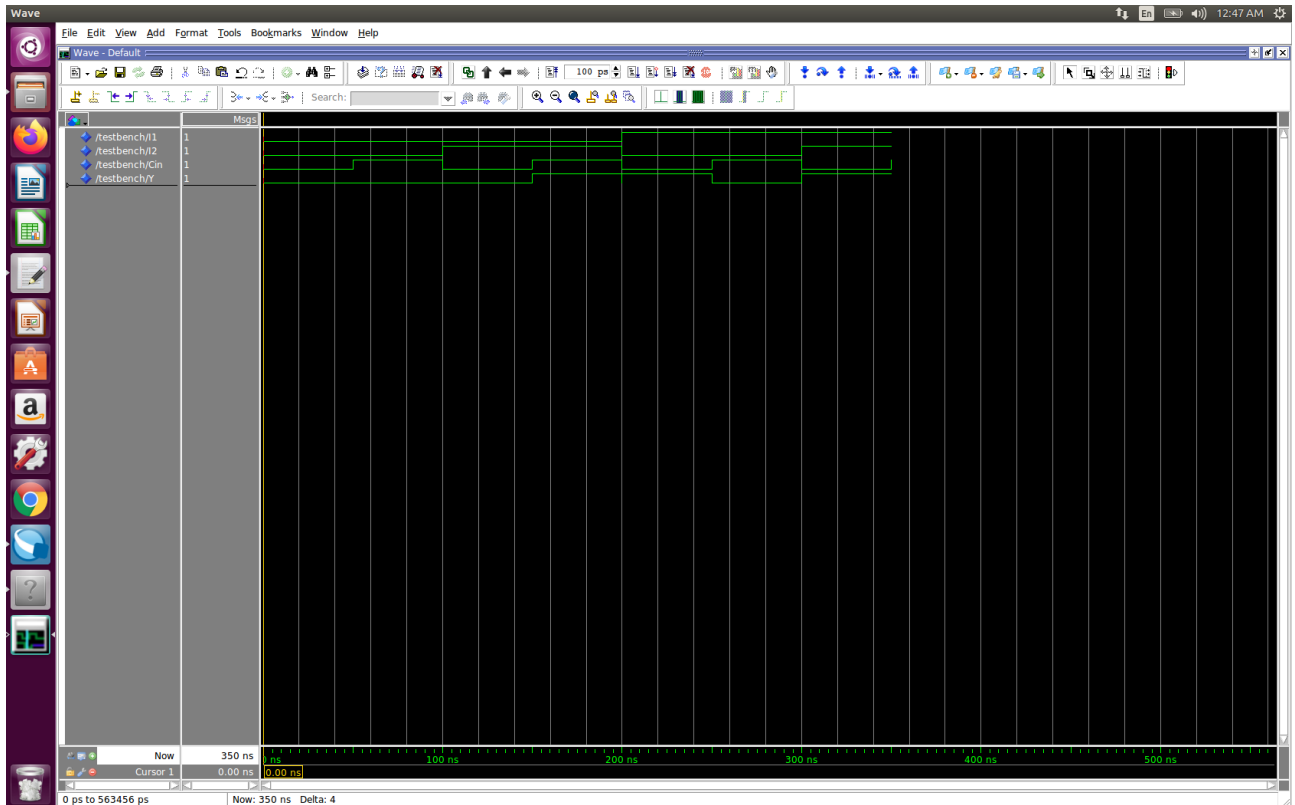


Simulations for HW1:

1. Mux simulation

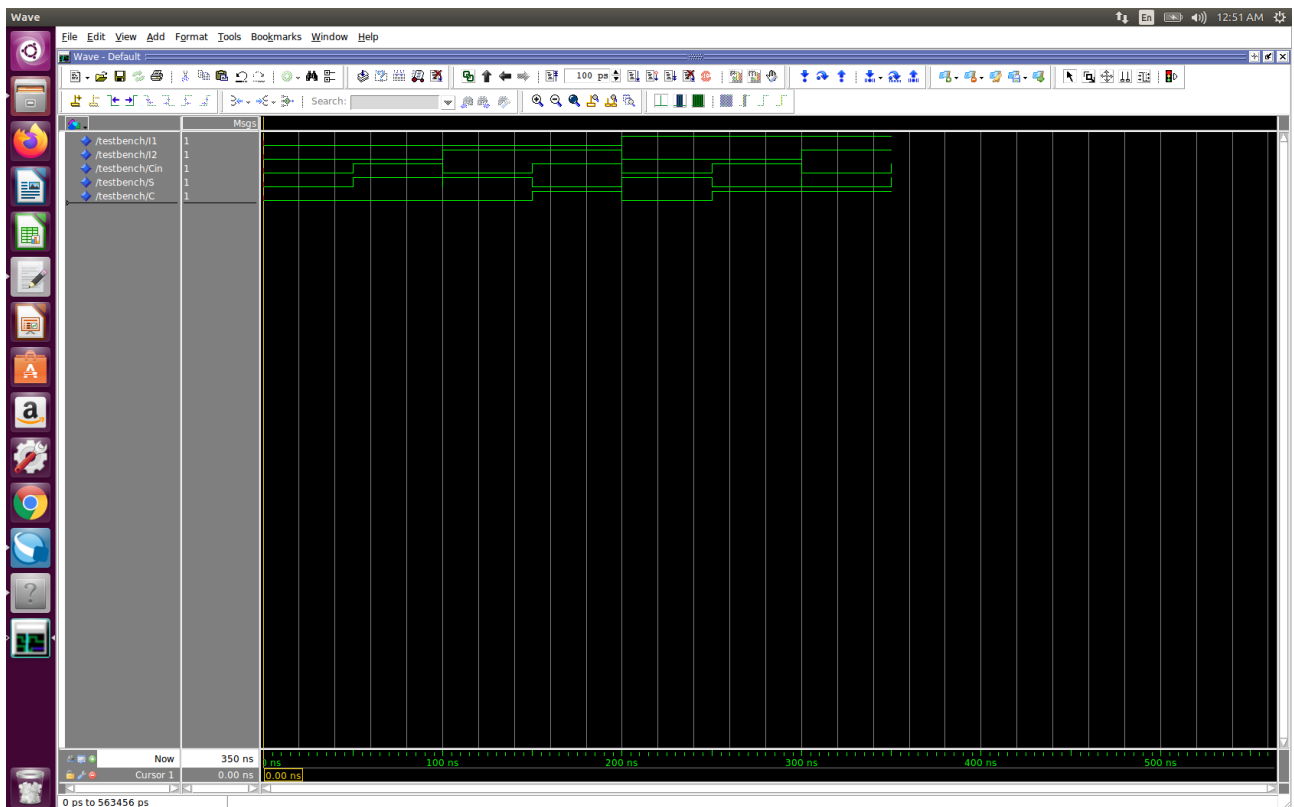


2. Fulladder simulation




Lab1 BDDs and simulations:


1.

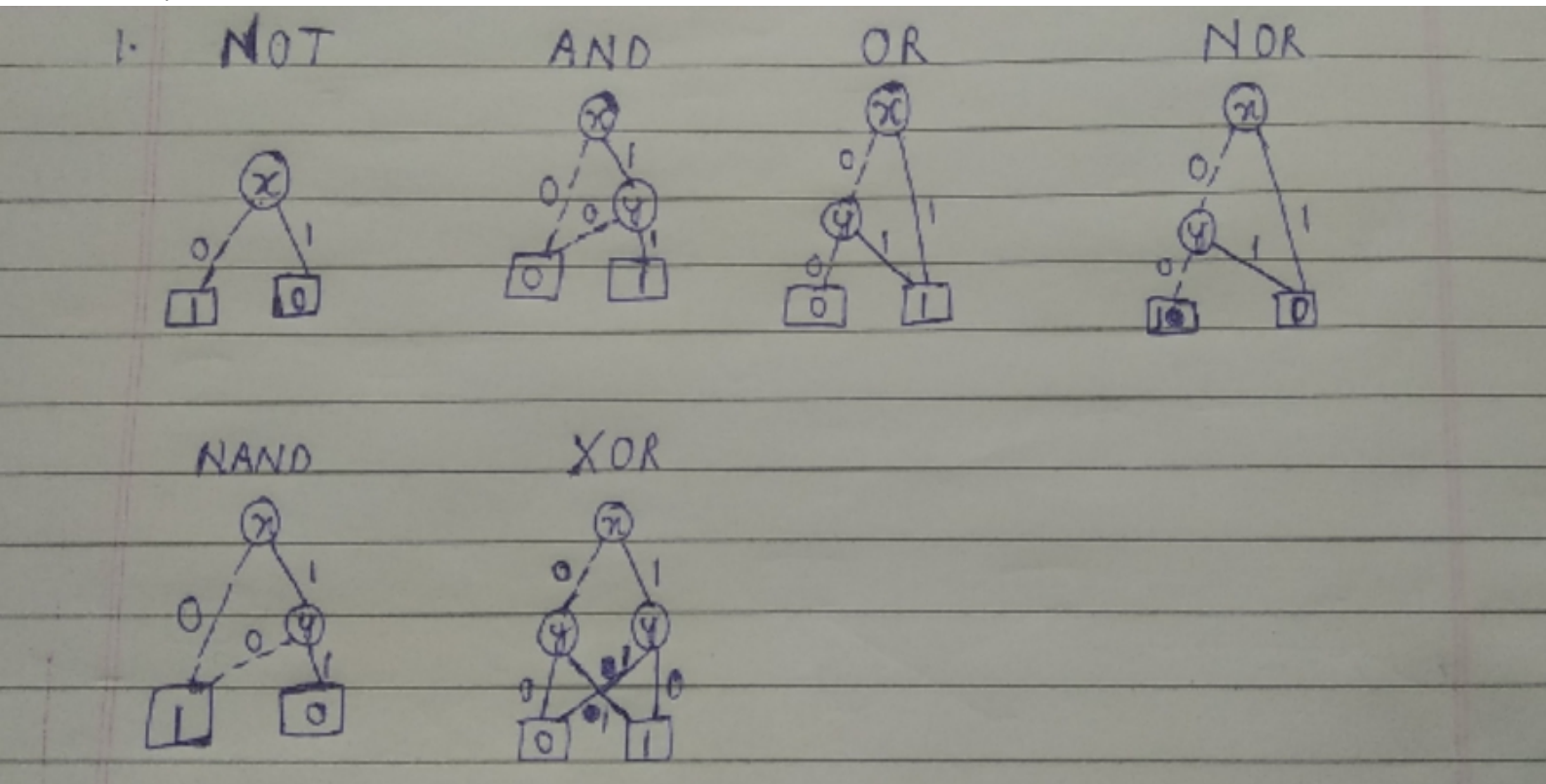


NOT simulation

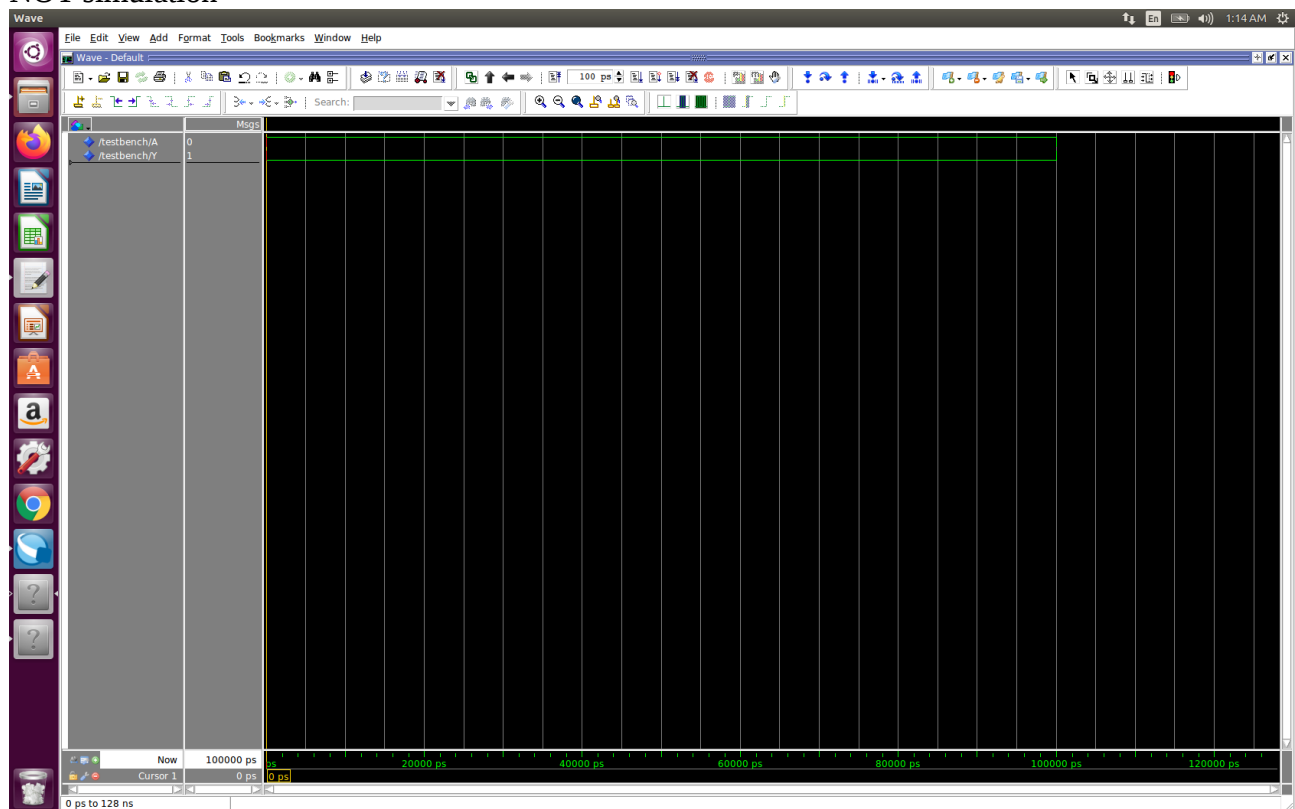


AND simulation

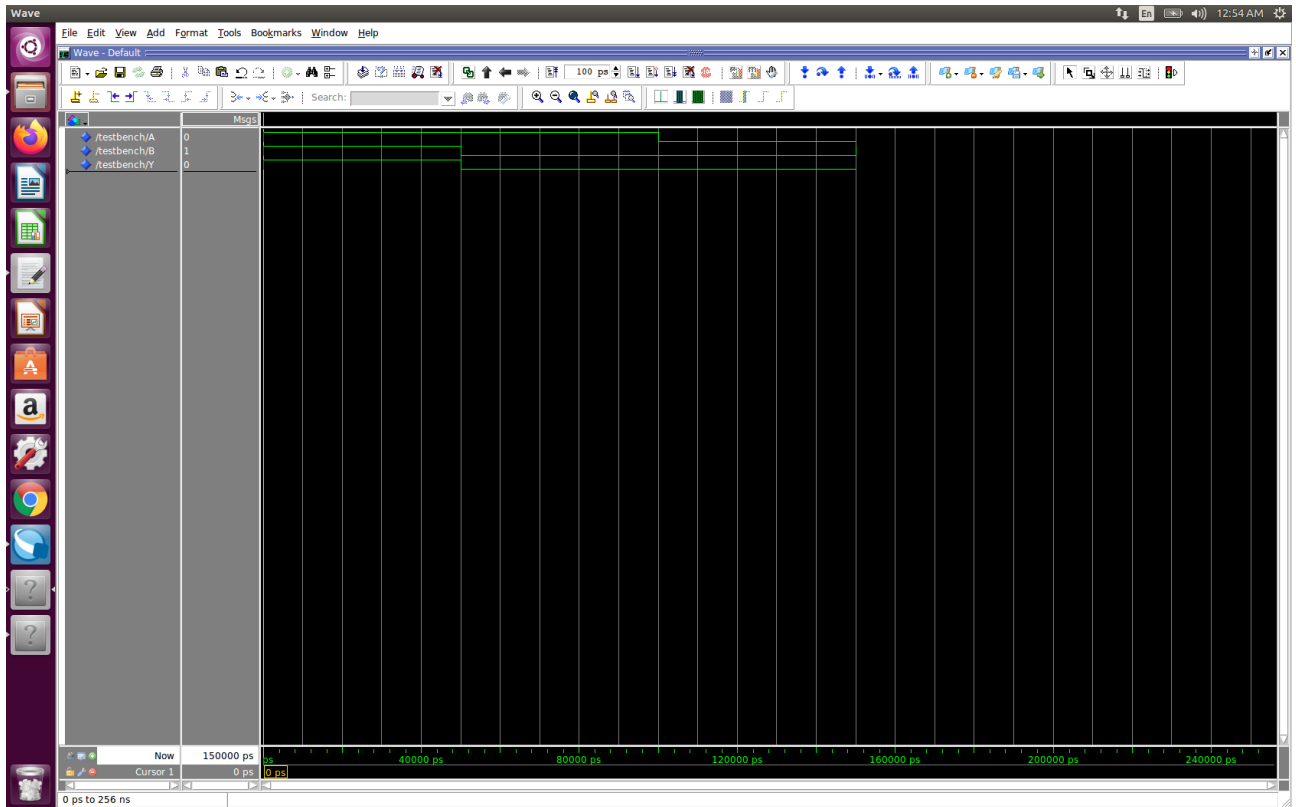


OR simulation

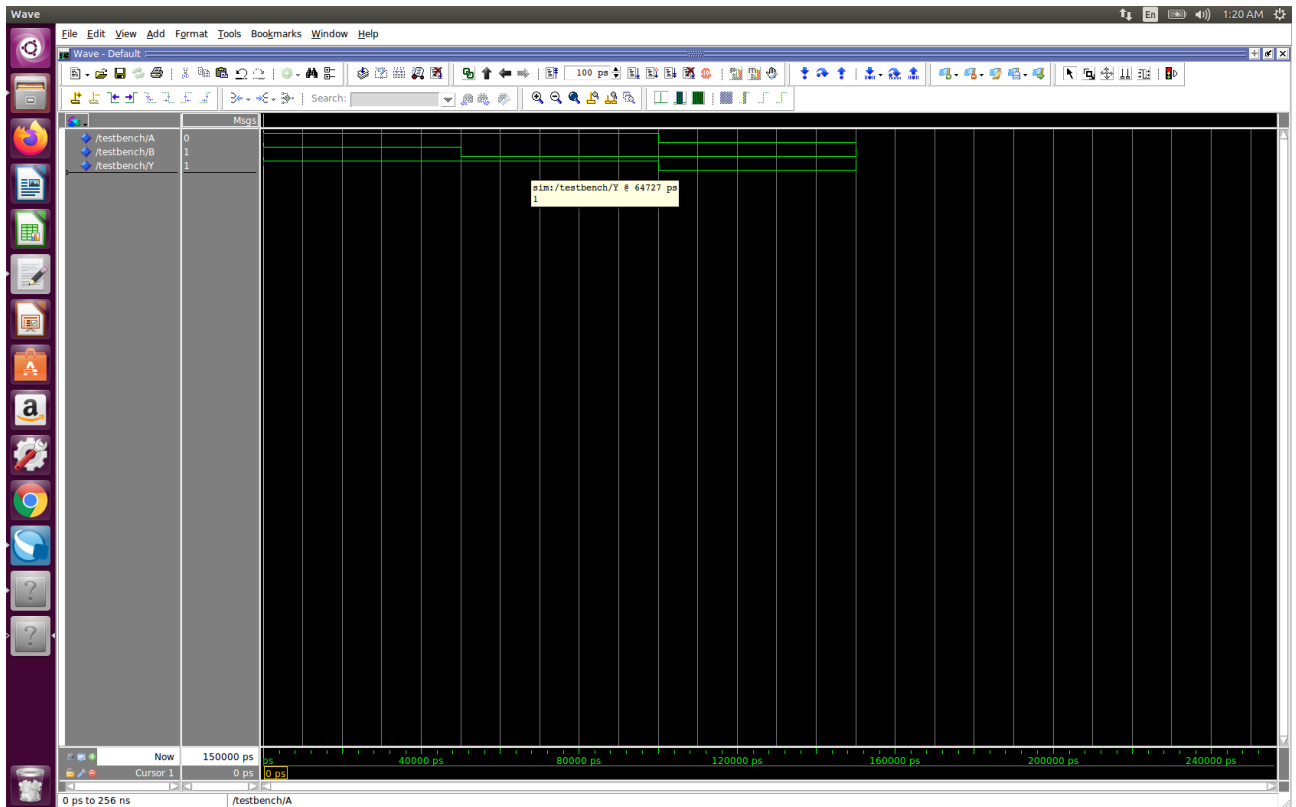


NOR simulation

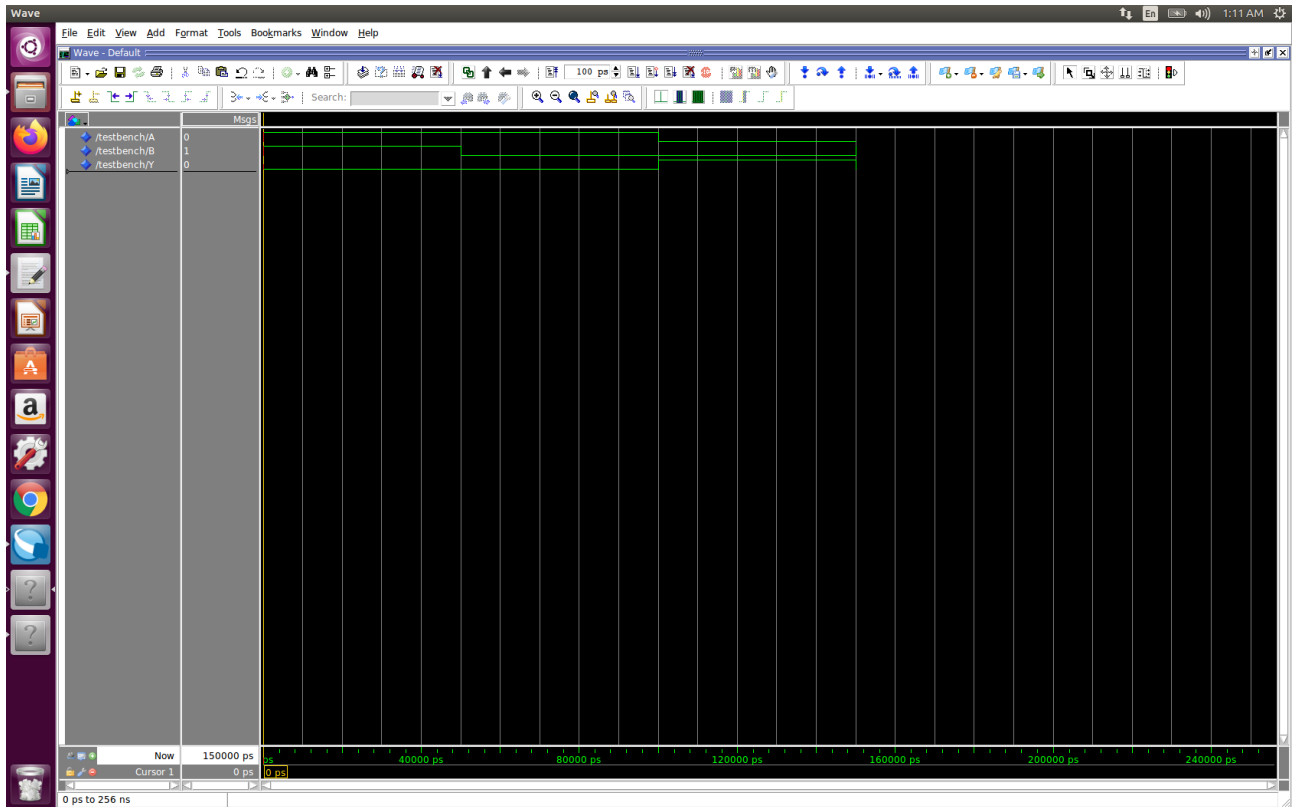

NAND simulation

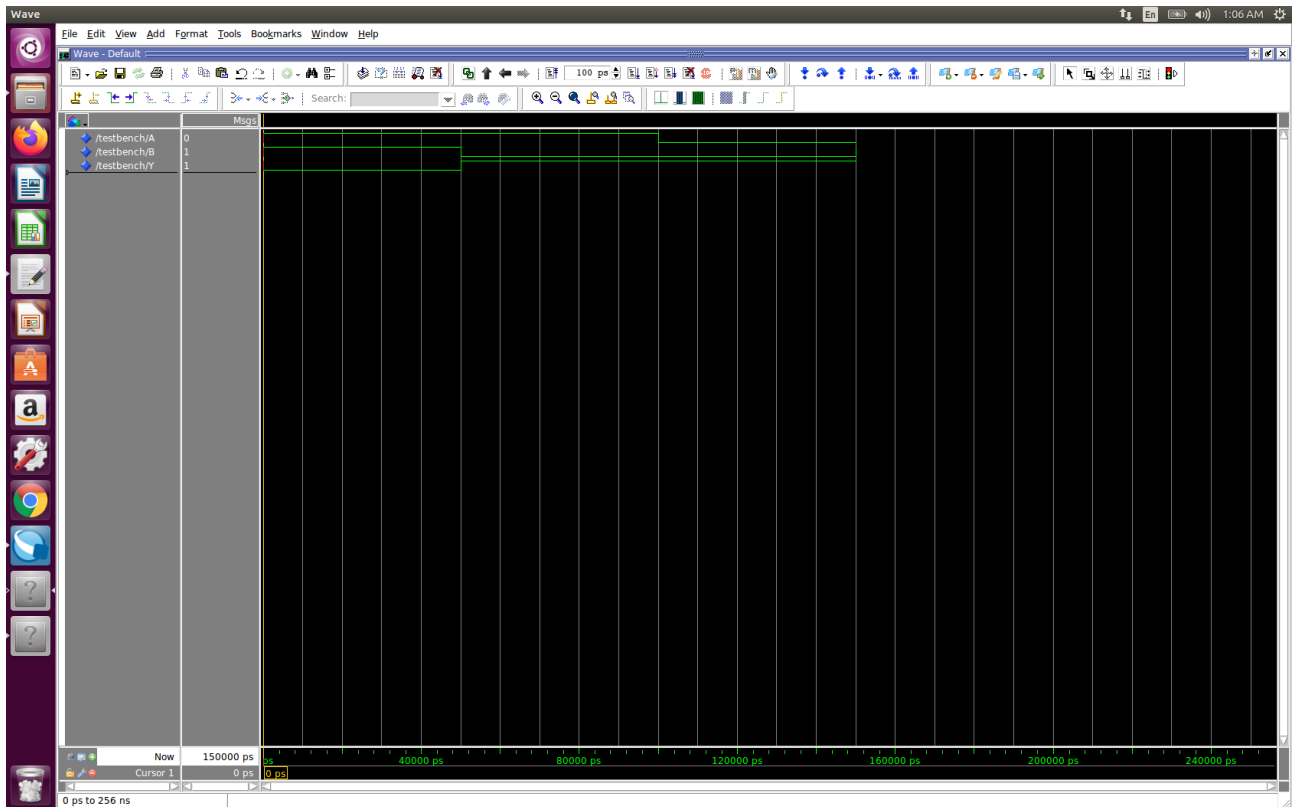


XOR

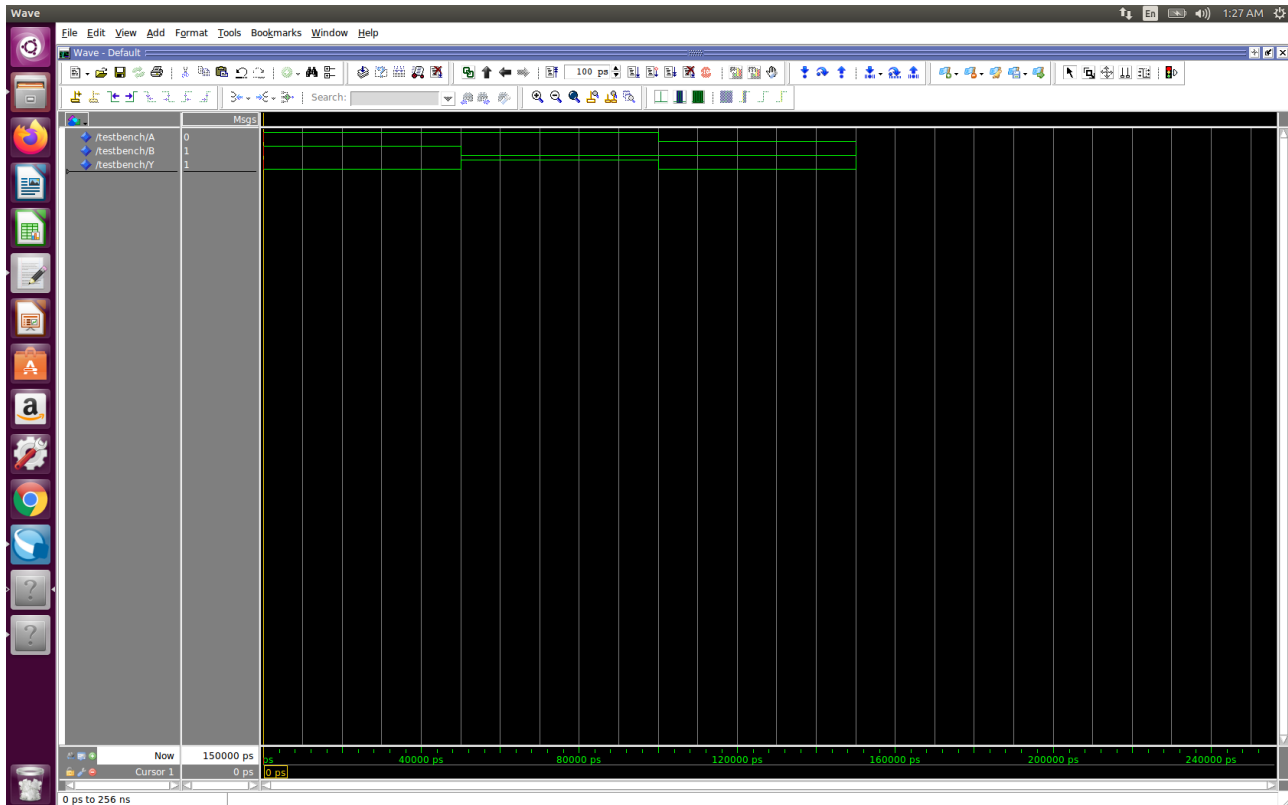



2.



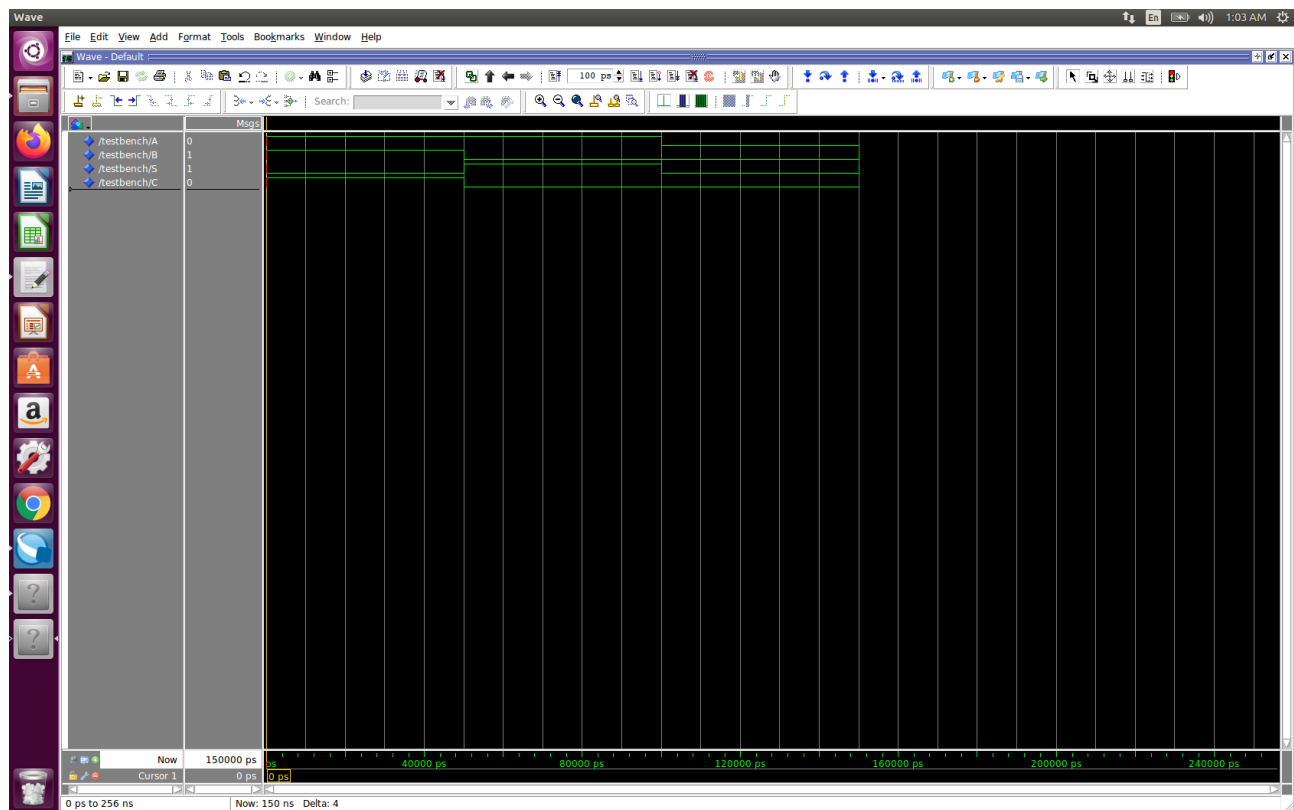

3.

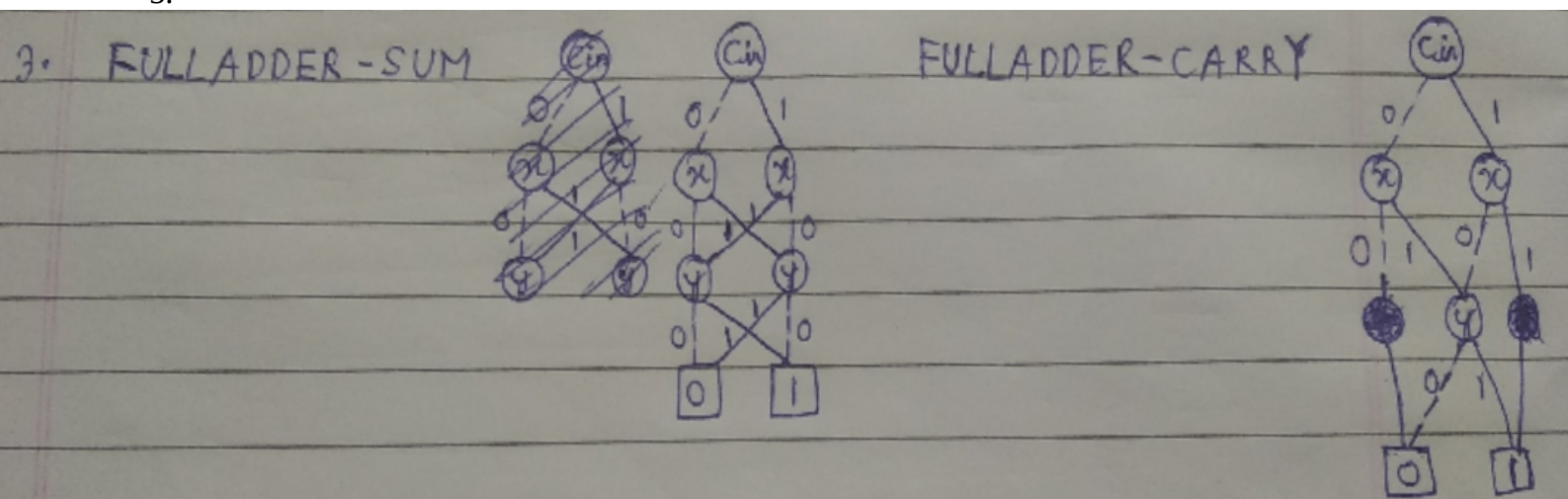

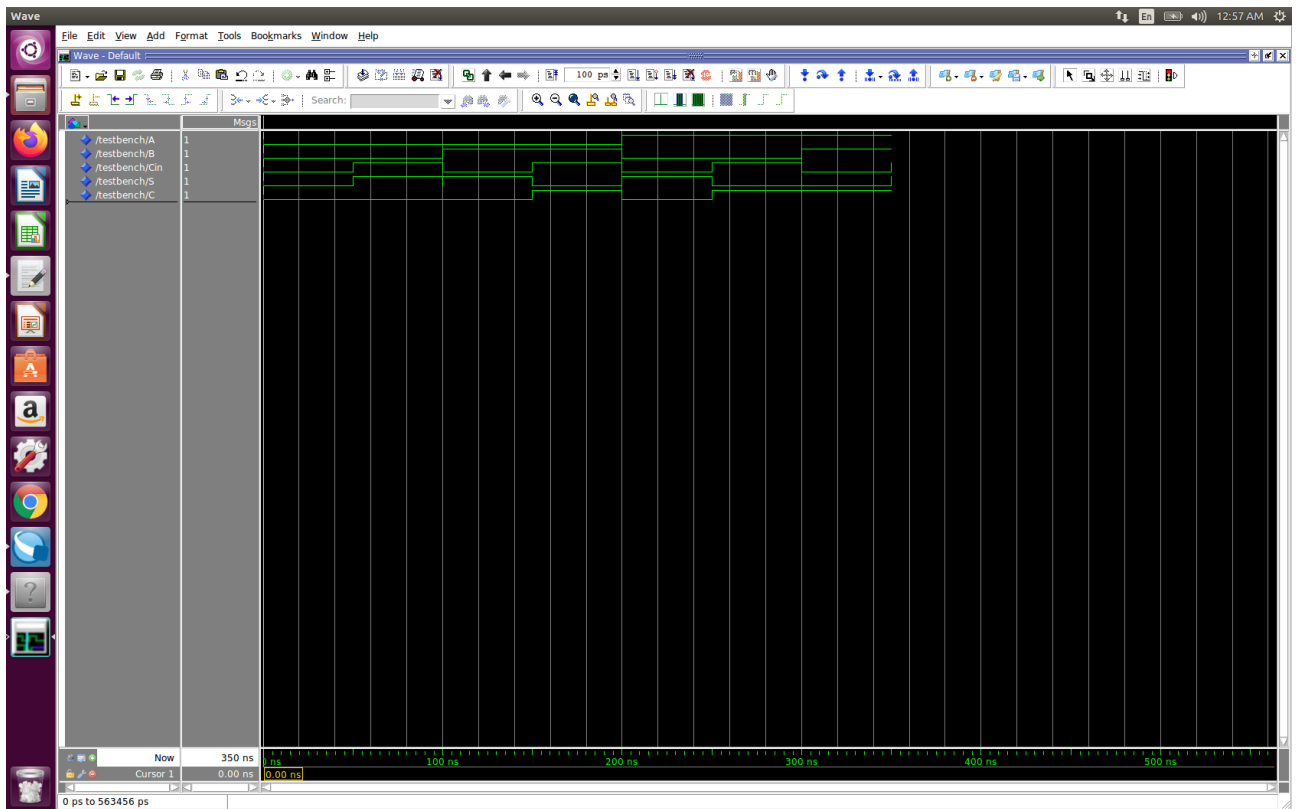

4.

