

## Lab 3-Homework

10-02-2020

CS 254-Digital Logic Design Lab

The following digital circuits must be designed using VHDL, and simulated and tested using Quartus.

The design should be **Behavioural**.

Q. Design a 4-bit arithmetic circuit which should have:

1. 4-bit adder-subtractor similar to the homework
2. 4-bit NAND logic function
3. 2-bit multiplier same as the homework

Inputs	Select line( $S_1S_0$ )	Function	Output
$A_{3-0}, B_{3-0}$	00	Adder	$Z_{4-0}$
$A_{3-0}, B_{3-0}$	01	Subtractor	$Z_{4-0}$
$A_{3-0}, B_{3-0}$	10	NAND	$Z_{3-0}$ (Rest zeros)
$A_{1-0}, B_{1-0}$	11	Multiplier	$Z_{3-0}$ (Rest zeros)

