

Lab 4-Classwork Part 1


19-02-2020

CS 254-Digital Logic Design Lab

14:00-16:55

The following digital circuits must be designed using VHDL, and simulated and tested using Quartus.

 Q1. (10marks) Design a 1x2 Demultiplexer and a 1x4 Demultiplexer.



Input	S ₀	AB
0	0	00
1	0	01
0	1	00
1	1	10


Input	S ₁	S ₀	ABCD
0	0	0	0000
1	0	0	0001
0	0	1	0000
1	0	1	0010
0	1	0	0000
1	1	0	0100
0	1	1	0000
1	1	1	1000

The trace file format for the design is as follows:

Input S₀ AB | Input S₁S₀ ABCD

Q2. (5marks) Design a 2x4 Decoder.

I ₁	I ₀	A	B	C	D
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

 


The trace file format for the design is as follows:

I₁I₀ ABCD

Q3. (5marks) Design a 4x2 Priority encoder.

En	A	B	C	D	O ₁	O ₀	V
0	x	x	x	x	x	x	0
1	0	0	0	0	x	x	0
1	0	0	0	1	0	0	1
1	0	0	1	x	0	1	1
1	0	1	x	x	1	0	1
1	1	x	x	x	1	1	1

 

The trace file format for the design is as follows:

EnABCD O₁O₀V